

中山大学本科生期末考试

考试科目：《数 字 电 路 》（A 卷）答案

学年学期：2017 学年第二学期

姓 名：_____

学 院/系：电子与信息工程学院

学 号：_____

考试方式：闭卷

年级专业：_____

考试时长：120 分钟

班 别：_____

警示

《中山大学授予学士学位工作细则》第八条：“考试作弊者，不授予学士学位。”


-----以下为试题，共 2 道大题，总分 100 分,考生请在答题纸上作答-----

一、填空题（共 25 小题，每个答案 2 分，共 50 分）

1. 10101010
2. 0.0101000
3. 011011
4. 11011
5. 1
6. $X = \overline{AB} + A\overline{B}$
7. $X = (\overline{A+B+C})(\overline{A+B+C})(A+B+C)$
8. AND
9. NAND
10. COMP A
11. Propagation delay 传输延迟时间
12. 不可重复触发
13. Astable multivibrator 振荡器
14. 2Hz
15. 8
16. 1000
17. Faster speed 速度快
18. EEPROM
19. word length 字长
20. 255
21. Dual slope ADC
22. R-2R Ladder DAC
23. NOT
24. ON OFF

二、分析设计题（共 4 小题，共 50 分）

1. Write the output expression for the circuit shown below, obtain the truth table according to the expression, and determine the logic function. (写出所示逻辑电路的输出表达式, 列出真值表, 并确定其逻辑功能) (8 points)

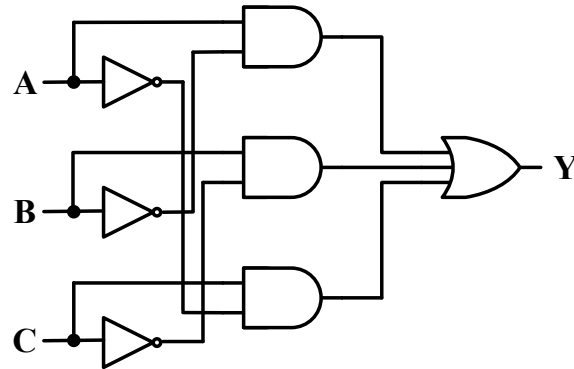

(Question. 1)

答案:

$$Y = A\bar{B} + B\bar{C} + \bar{A}C$$

(2 points)


Input			
A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

(4 points)

Logic function: The output is high when the inputs are different.

(2 points)

2. Design a 1 bit full subtractor (设计一个一位全减器来计算 $A-B-C$), which computes $A-B-C$, where C is the borrow from the next less significant digit (其中 C 是来自低位的借位). It produce a difference D and a borrow from the next more significant bit P . (它将得到差 D 和对高位的借位)
- (a) Implement the full subtractor by gates(write down the logic functions for the D and P , don't draw the circuit diagram) (采用逻辑门实现这个全减器, 只需写出 D 和 P 的逻辑表达式, 不需要画出电路图) (8 points)
- (b) Implement the full subtractor by 74LS153 multiplexer and some gates (draw the circuit diagram). 74HC153 has two identical 4-input multiplexers which select two bits of data from up to four sources according to common data select inputs. (采用 74LS153 和逻辑门来实现这个全减器, 需画出具体电路图, 其中 74HC153 包含两个四输入多路复用器) (4 points)

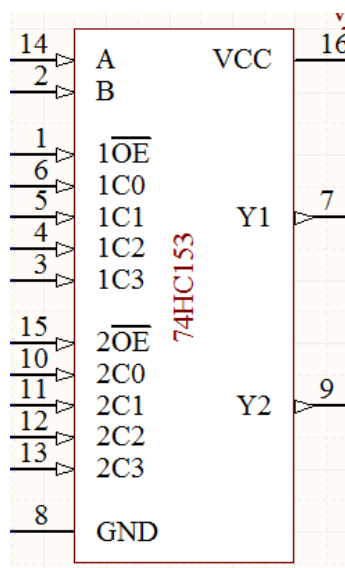

(Question. 2)

答案:

The truth table for the full subtractor is as follows:


a	b	c	p	d
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

(4 points)

$$d = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc$$


$$p = \bar{a}\bar{b}c + \bar{a}b\bar{c} + \bar{a}bc + abc = b\bar{c} + \bar{a}c + \bar{a}b$$

(4 points)

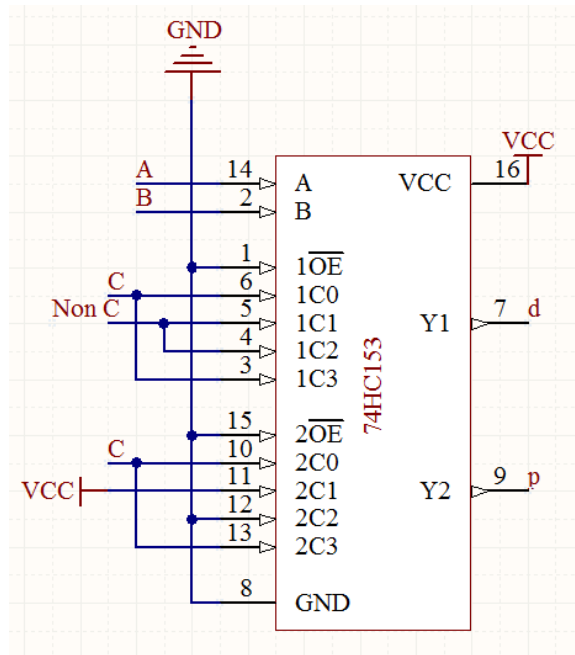

(4 points)

3. Determine the logic function of the circuit sketched below. (确定下图所示电路的逻辑功能) The detailed procedure is required. (需给出具体过程) (14 points)

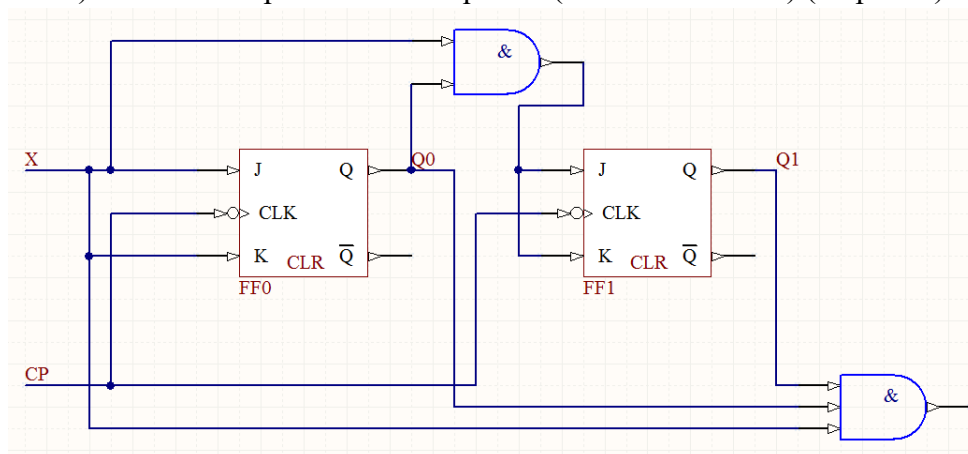

(Question. 3)

答案:

Excitation expression:

$$\begin{cases} J_0 = K_0 = X \\ J_1 = K_1 = XQ_0^n \end{cases}$$

State expression:

$$\begin{cases} Q_0^{n+1} = X \cdot \overline{Q_0^n} + \overline{X} \cdot Q_0^n \\ Q_1^{n+1} = X \cdot Q_0^n \cdot \overline{Q_1^n} + \overline{X} \cdot Q_0^n \cdot Q_1^n \end{cases}$$


Output expression:

$$Z = X \cdot Q_0^X \cdot Q_1^X$$

(6 points)

	X=0	X=1
00	00 / 0	01 / 0
01	01 / 0	10 / 0
10	10 / 0	11 / 0
11	11 / 0	00 / 1

(4 points)

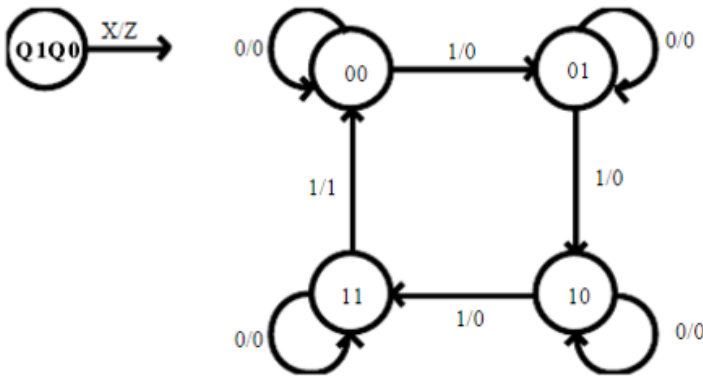

Logic function:

When X=0, the circuit remains unchanged.

When X=1, the circuit is a four bits synchronous binary counter. (4 points)

4. Design a synchronous modulus-5 counter using D flip-flops and necessary gates(用 D 触发器和必要逻辑门设计一个同步模-5 计数器). The counter is required to go through the following sequence: 0->2->4->1->3->0->.... (要求计数器产生以下时序: 0, 2, 4, 1, 3, 0,...) The detailed procedure is required. (需给出具体过程). (16 points)

答案:

$Q_2^n Q_1^n Q_0^n$	$Q_2^{n+1} Q_1^{n+1} Q_0^{n+1}$	Z
000	010	0
010	100	0
100	001	0
001	011	0
011	000	1

(6 points)

$$Q_2^{n+1} = D_2, Q_1^{n+1} = D_1, Q_0^{n+1} = D_0$$

The K-map

Q2 \ Q1Q0	00	01	11	10
0	0	0	0	1
1	0	X	X	X

$$D_2 = Q_1 \bar{Q}_0$$

Q2 \ Q1Q0	00	01	11	10
0	1	1	0	0
1	0	X	X	X

$$D_1 = \bar{Q}_1 \cdot \bar{Q}_2$$

Q2 \ Q1Q0	00	01	11	10
0	0	1	0	0
1	1	X	X	X

$$D_0 = Q_2 + \bar{Q}_1 Q_0$$

Q2 \ Q1Q0	00	01	11	10
0	0	0	1	0
1	0	X	X	X

$$Z = Q_1 Q_0$$

(4 points)

Excitation expression.

$$D_2 = Q_1 \cdot \bar{Q}_0, \quad D_1 = \bar{Q}_2 \cdot \bar{Q}_1, \quad D_0 = Q_2 + \bar{Q}_1 \cdot Q_0, \quad Z = Q_1 Q_0 \quad (4 \text{ points})$$

Check self boot

$Q_2^n Q_1^n Q_0^n$	$Q_2^{n+1} Q_1^{n+1} Q_0^{n+1}$	Z
---------------------	---------------------------------	---

000	010	0
010	100	0
100	001	0
001	011	0
011	000	1
101	001	0
110	101	0
111	001	1

The circuit can self boot.

(2 points)